

## DC Circuits

As you work through the steps in the lab procedure, record your experimental values and the results on this worksheet. Use the exact values you record for your data to make later calculations.

### Procedure A: Reading the color code of unknown resistors

Complete the data table below.

**Data Table 1**

Resistor	Band #1		Band #2		Band #3		Resistance ( $\Omega$ )
	color	value	color	value	color	value	
1							
2							

**CHECKPOINT 1:** Ask your TA to check your reading of the color code.

**Procedure B: Experimentally determining the resistance of resistor 1****CHECKPOINT 2: Ask your TA to check your circuit and multimeter settings.**Complete the data table below for  $R_1$ .**Data Table 2**

<b>Trial #</b>	<b><math>\Delta V</math> (V)</b>	<b>current (A)</b>
<b>1</b>		
<b>2</b>		
<b>3</b>		
<b>4</b>		
<b>5</b>		

What is the experimental value of  $R_1$  (from your plot of voltage versus current)?What is the percent error between the experimental and accepted values of  $R_1$ ?

Is your measured resistance value in close agreement with the accepted value from Data Table 1?  
(Consider your percent error exactly as you have entered it.)

**CHECKPOINT 3:** Ask your TA to check your chart, calculations, and Excel graph before proceeding.

### Procedure C: Experimentally determining the resistance of resistor 2

Complete the data table below for  $R_2$ .

**Data Table 3**

Trial #	$\Delta V$ (V)	current (A)
1		
2		
3		
4		
5		

What is the experimental value of  $R_2$  (from your plot of voltage versus current)?

What is the percent error between the experimental and accepted values of  $R_2$ ?

Does your measured resistance value agree with the expected value within the measured tolerance? (Consider your percent error exactly as you have entered it.)

**CHECKPOINT 4:** Ask your TA to check your chart, calculations, and Excel graph before proceeding.

### Procedure D: Series Arrangement

**CHECKPOINT 5:** Ask your TA to check your circuit before proceeding.

Complete the data table below for the series arrangement. Take  $\Delta V_{\text{meas}}$  to be the voltage across the combination of resistors.

**Data Table 4**

Trial #	$\Delta V_{\text{meas}}$ (V)	current (A)	$\Delta V_1$ across $R_1$ (V)	$\Delta V_2$ across $R_2$ (V)	$\Delta V_{\text{calc}}$ across $(R_1 + R_2)$ (V)	% difference
1						
2						
3						
4						
5						

What is the experimental value of the equivalent resistance for the series combination (from your plot of voltage versus current)?

What is the calculated value of the equivalent resistance for the series combination using the values from Data Table 1?

What is the percent error between the experimental value and calculated value of  $R_s$ ?

Is your measured resistance value in close agreement with the calculated value? (Consider your percent error exactly as you have entered it.)

Compare  $\Delta V_{\text{calc}}$  with  $\Delta V_{\text{meas}}$ . Do the voltage drops across the individual resistances add up to the total voltage drop across the combination for each of the five readings? (Consider your percent differences in Data Table 4 exactly as you have entered them.)

<b>CHECKPOINT 6:</b> Ask your TA to check your chart, calculations, and Excel graph before proceeding.
--

## Procedure E: Parallel Arrangement

**CHECKPOINT 7:** Ask your TA to check your circuit before proceeding.

**CHECKPOINT 8:** Enter your data for Trial 1 in Data Table 5 below. Ask your TA to check your chart, calculations, and Excel graph before proceeding to the rest of Data Table 5.

Complete the data table below for the parallel arrangement. Take  $I_{\text{meas}}$  to be the current from the power supply.

**Data Table 5**

Trial #	$\Delta V_{\text{meas}}$ (V)	$I_{\text{meas}}$ (A)	$I_1$ for $R_1$ (A)	$I_2$ for $R_2$ (A)	$I_{\text{calc}}$ for $(R_1 + R_2)$ (A)	% difference
1						
2						
3						
4						
5						

What is the experimental value of the equivalent resistance for the parallel combination (from your plot of voltage versus current)?

What is the calculated value of the equivalent resistance for the parallel combination using the values from Data Table 1?

What is the percent error between the experimental value and calculated value of  $R_p$ ?

Is your measured resistance value in close agreement with the calculated value? (Consider your percent error exactly as you have entered it.)

Compare  $I_{\text{calc}}$  with  $I_{\text{meas}}$ . Do the currents flowing through the individual resistances add up to the total current flowing in the circuit for each of the five readings? (Consider your percent differences in Data Table 5 exactly as you have entered them.)